 


Answer all the questions.

1. Draw the logic gates represented by the Karnaugh Map below. Show your working.

[4]

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	1	1	0	0
	11	0	0	1	1
	10	0	0	1	1



2. An electronics engineer needs a circuit with the following logic.

$$(A \wedge B) \vee (\neg A \wedge B) \vee (\neg C \wedge \neg D)$$

Complete and use the Karnaugh map below to simplify the expression above.

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

		AB			
		00	01	11	10
CD	00	1	1	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

Simplified expression:

$$F = B + \overline{C}\overline{D}$$

---

[4]

- 3(a). Draw an XOR gate.



[1]

- (b). Explain the difference in the function of OR and XOR gates.

= OR can be seen as AND/OR connector. One or both choices can be true or chosen. XOR, on the other hand, could be described as real OR. Only one of both choices can be true (or chosen)

---

[2]

4. A NAND gate and its truth table are shown in Fig. 10.1.

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0


 


Fig. 10.1

 Draw a set of gates equivalent to a NAND gate, but built only of AND, OR and NOT gates.



[2]

END OF QUESTION PAPER

[Type here]